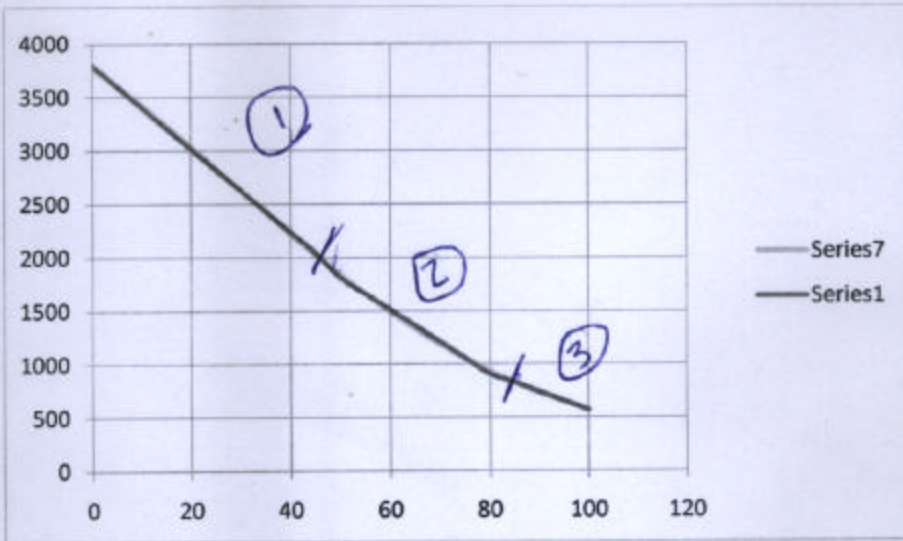


# Linearized Thermistors #2


Sept 27, '10

Req  
A-B  
Ω



FIG#4

Tc °C

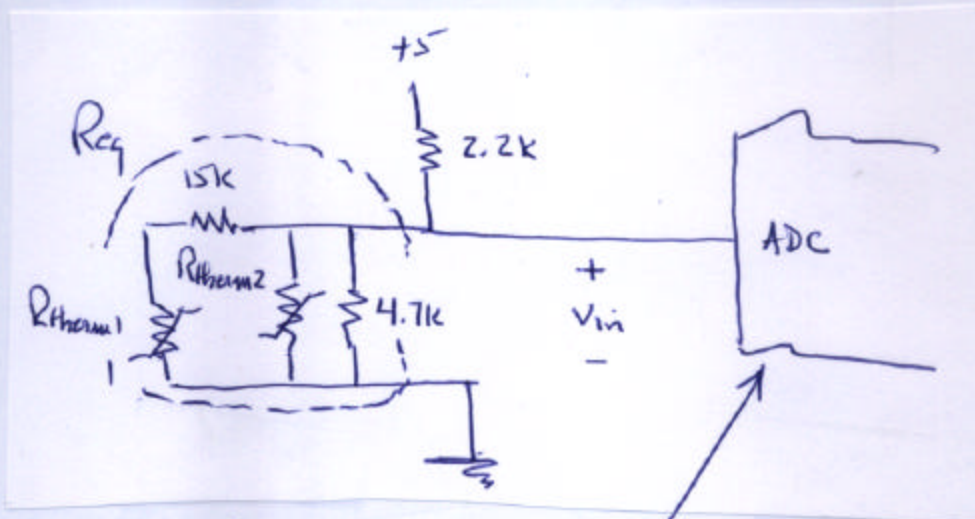

FIG#5

PCAXE or  
ARDUINO or  
SIMILAR